Christopher Lall In class lab assignment 1 – BUZZER CSc 34300 & CSc 34200 Due 2/16/2022

Table of Contents

Objective	3
Buzzer	3
4 to 1 Mux	7
Explanation	
Conclusion	٠٠ ک

Objective

The objective of this lab is to simulate the Buzzer and 4to1 Mux code and verify its accuracy with the truth tables.

Buzzer

Screenshots:

```
library IEEE;
use IEEE.std_logic_1164.all;
1234567891112345167892122345678990123345678990412344434
     □entity Lall_Christopher_FEB16_2022_BUZZER is
            port (DOOR, IGNITION, SBELT: in std_logic;
                   WARNING: out std_logic);
            end Lall_Christopher_FEB16_2022_BUZZER;
     □architecture structural of Lall_Christopher_FEB16_2022_BUZZER is
                   -- Declarations
     component Lall_Christopher_AND2
                         port (in1, in2: in std_logic;
                               out1: out std_logic);
                   end component;
                   component Lall_Christopher_OR2
                         port (in1, in2: in std_logic;
                               out1: out std_logic);
                   end component;
                   component Lall_Christopher_NOT1
                         port (in1: in std_logic;
                               out1: out std_logic);|
                   -- declaration of signals used to interconnect gates
       signal DOOR_NOT, SBELT_NOT, B1, B2: std_logic;
```

Figure 1. Code for Buzzer file

Figure 2. Code for AND2

Figure 3. Code for NOT1

```
Library IEEE;
use IEEE.std_logic_1164.all;

Dentity Lall_christopher_OR2 is

Dentity Lall_christopher_OR2 is

Dentity Lall_christopher_OR2;

Lend Lall_christopher_OR2;

Dentity Lall_christopher_OR2;

Dentity Lall_christopher_OR2;

Dentity Lall_christopher_OR2;

Dentity Lall_christopher_OR2 is

Dentity Lall_christopher_OR2 i
```

Figure 4. Code for OR2

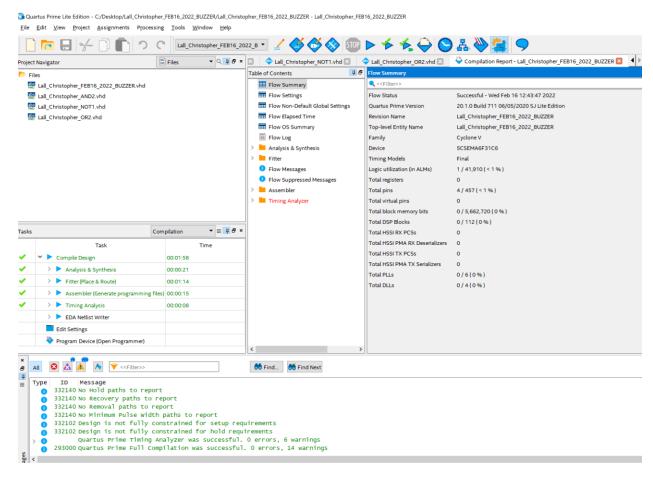


Figure 5. Compilation Report in Quartus

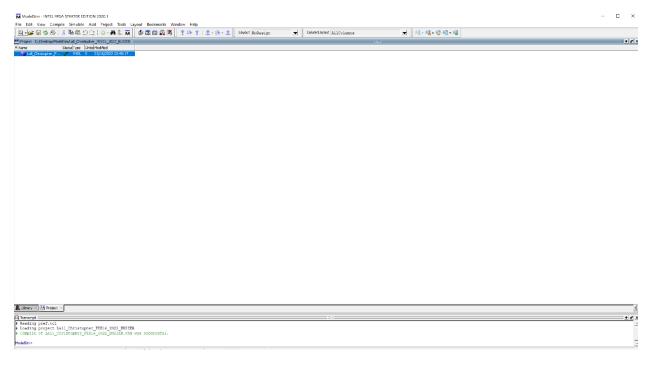


Figure 6. Compilation in ModelSim

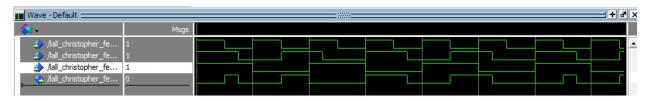


Figure 7. Waveform in ModelSim



Figure 8. Verification of an example

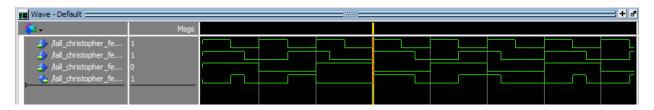


Figure 9. Another example

4 to 1 Mux

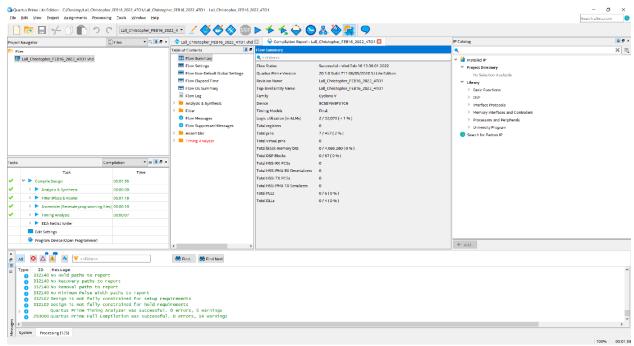


Figure 10. Compile in Quartus for Mux



Figure 11. Compilation in ModelSim

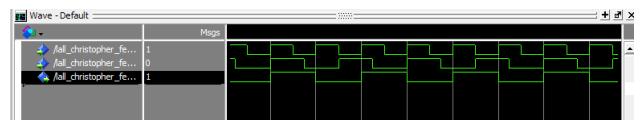


Figure 12. Waveform of 4:1 Mux



Figure 13. Example of MSGS

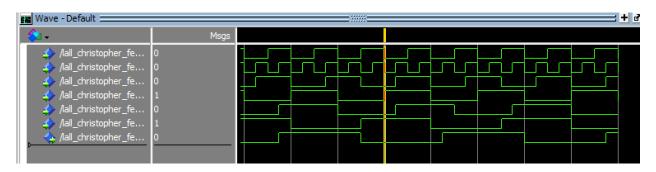


Figure 14. Verification example

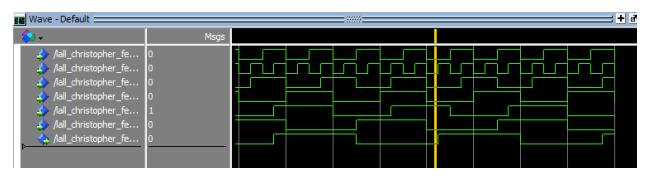


Figure 15. Verification, s1, s0, a, output 0

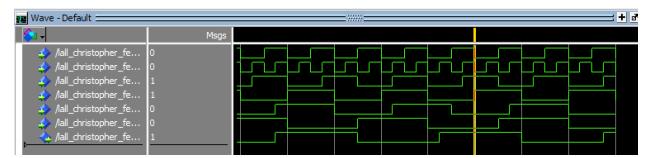


Figure 16. Verification s0 0 s1 1 a 1 output 1

Explanation

The screenshots demonstrate how I was able to reach my goal of compiling the code and then importing it to modelsim to get waves.

Conclusion

From doing the tutorial from the previous week, I was able to compile and get waveforms from ModelSim.