

Cs 343  
Spring 2022  
Adder Lab 3A

**TASKS TO DO:**

1. Design in VHDL Half adder using two processes
2. Design 1-bit Full-adder using Half adder as a component
3. Design N=4 bit adder using 1bit Full adder as a component
4. Design N=4 bit a add/sub component that performs addition when the operations code=0, and subtraction when the operations code=1
5. Create a package where you put all components for future use( Your last name is part of package name)
6. Design N – bit add-sub unit **using behavioral VHDL model**
7. You have to design a circuit to output OVERFLOW , ZERO, NEGATIVE flags for N-bit add/sub.
8. Verify all your designs in simulation using waveforms in ModelSim for N=4, and N=32 bits using Most positive, Most negative integer as a first operand, and integers 1 and/or 2 as a second operand. You have to demonstrate that flags are set correctly in appropriate cases.
9. Create N-bit adder/subtractor unit using lpm and compare waveforms with your design
10. Create a Test-Bench file in vhdl to test Add\_SUB unit for n=16 bits. Please demonstrate that the test-bench detects an error (intentionally created) in your design and prints out simulation time, expected operand 1 and operand result value, actual result value, and values of operand 1 and operand 2 that caused the error.

**Complete REPORT, VIDEO IS REQUIRED FOR THIS EXERCISE.**

Cs 343  
Spring 2022  
Adder Lab 3A

**What to Submit:**

1. VHDL code for tasks 1,2,3,4,5 printout
2. VHDL code for tasks 6,7 printout
3. Waveforms for task 8 in Model-Sim for N=4, and N=32

In waveforms You must use the following operands


- a. Most Positive N bit integer + 1
- b. Most Positive N bit integer - 1
- c. Most Negative N bit integer + 1
- d. Most Negative N bit integer - 1
- e. Most Positive N bit integer- Most Negative N bit integer
- f. Most Positive N bit integer+ Most Negative N bit integer
- g. Most Positive N bit integer- Most Positive N bit integer

The output waveform signal values have to be in HEX, all flag values have to be shown in each case. For each case a-g you have to give a one sentence explanation.

4. VHDL code for task 9. and waveforms for operand cases 3a, 3b, ...,3g.
5. Task 10: Printout of two simulations: 1. that demonstrates error was detected and printouts all parameters described in Task 10, and 2. after the code was corrected the printout is no errors.

**6. WHEN TO SUBMIT? March 6, 11:00PM. Thank you for your efforts.**


# HALF-Adder

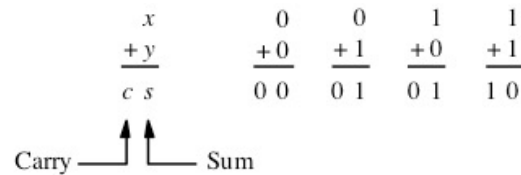


(a) The four possible cases

$x \quad y$		Carry $c$	Sum $s$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 


(c) Circuit

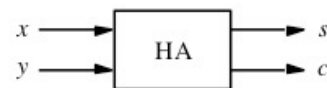


(d) Graphical symbol

# Full Adder Circuit

 


(a) Block diagram

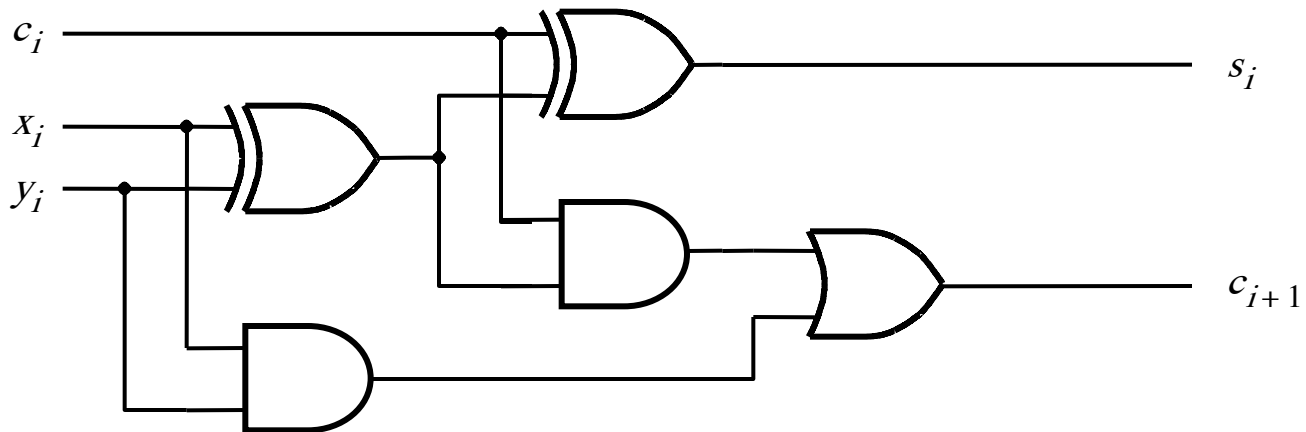

(b) Detailed diagram
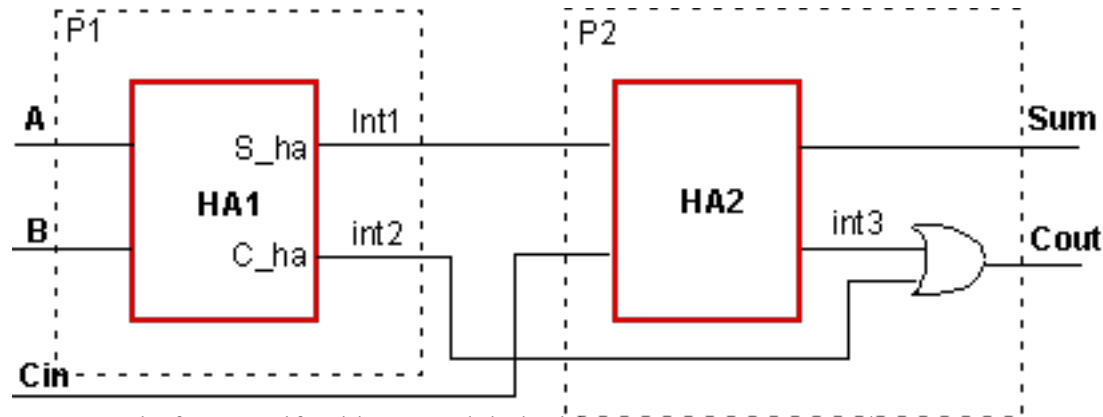
## Behavioral Modeling of an adder : Sequential Statements



Full Adder composed of two Half Adders, modeled with two processes P1 and P2.

```

library ieee;
use ieee.std_logic_1164.all;
entity FULL_ADDER is
    port (A, B, Cin : in std_logic;
          Sum, Cout : out std_logic);
end FULL_ADDER;


architecture BEHAV_FA of FULL_ADDER is
    signal int1, int2, int3: std_logic;
begin
    -- Process P1 that defines the first half adder
    P1: process (A, B)
        begin
            int1<= A xor B;
            int2<= A and B;
        end process;
    -- Process P2 that defines the second half adder and the OR -- gate
    P2: process (int1, int2, Cin)
        begin
            Sum <= int1 xor Cin;
            int3 <= int1 and Cin;
            Cout <= int2 or int3;
        end process;
end BEHAV_FA;

```

Of course, one could simplify the behavioral model significantly by using a single process.

Design N-Bit adder/SUB using VHDL

# An 4-bit ripple-carry adder

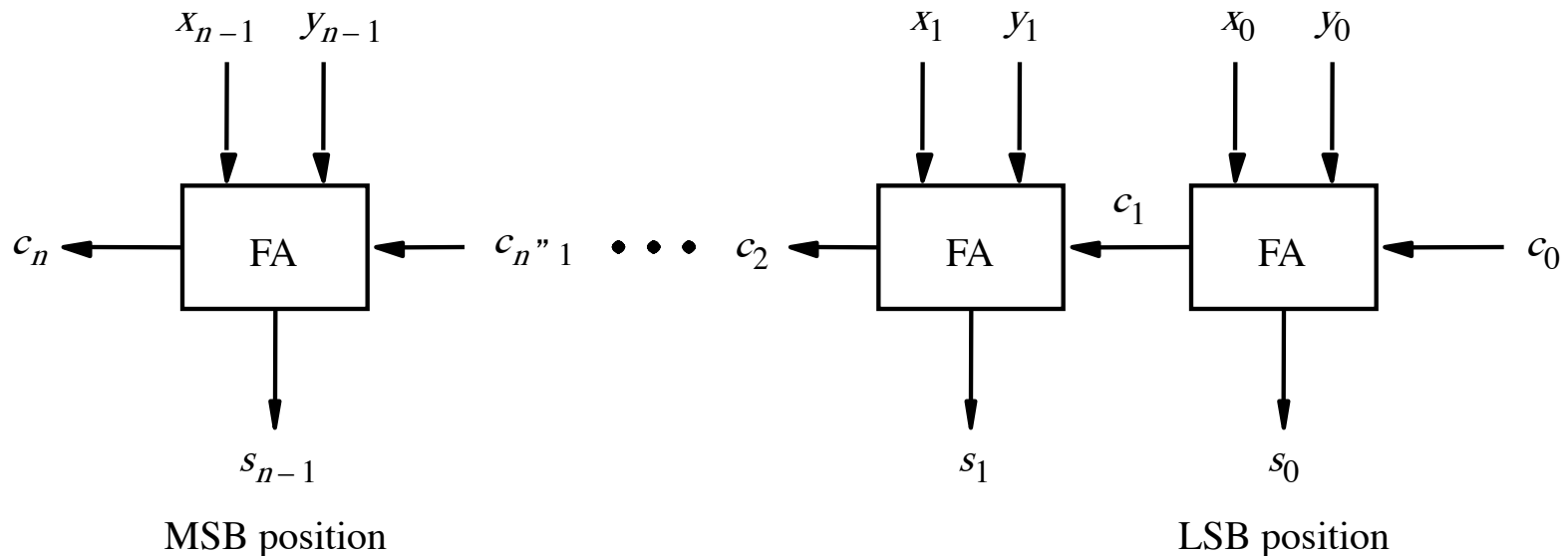

Denote by  $\Delta t$  time 1-Bit Full adder computes addition of two bits and carry.


*Question: How much time it takes to compute the sum of two 4 bits words ?*

# SUBTRACTOR FROM ADDER

BORROW 10-1 = 1  
↓

1101	-3	1101
-	-	+
1111	-1	0001
-----	-----	-----
1110	-2	1110

# Adder/Subtractor Unit

 


Add/Sub control is =1 then the output of the XOR gate is inverted Y (1's complement of Y).

$C_0=1$  in the case of subtraction we need to add 1 to form 2's complement of Y.

Recall: XOR performs module 2 operation!!


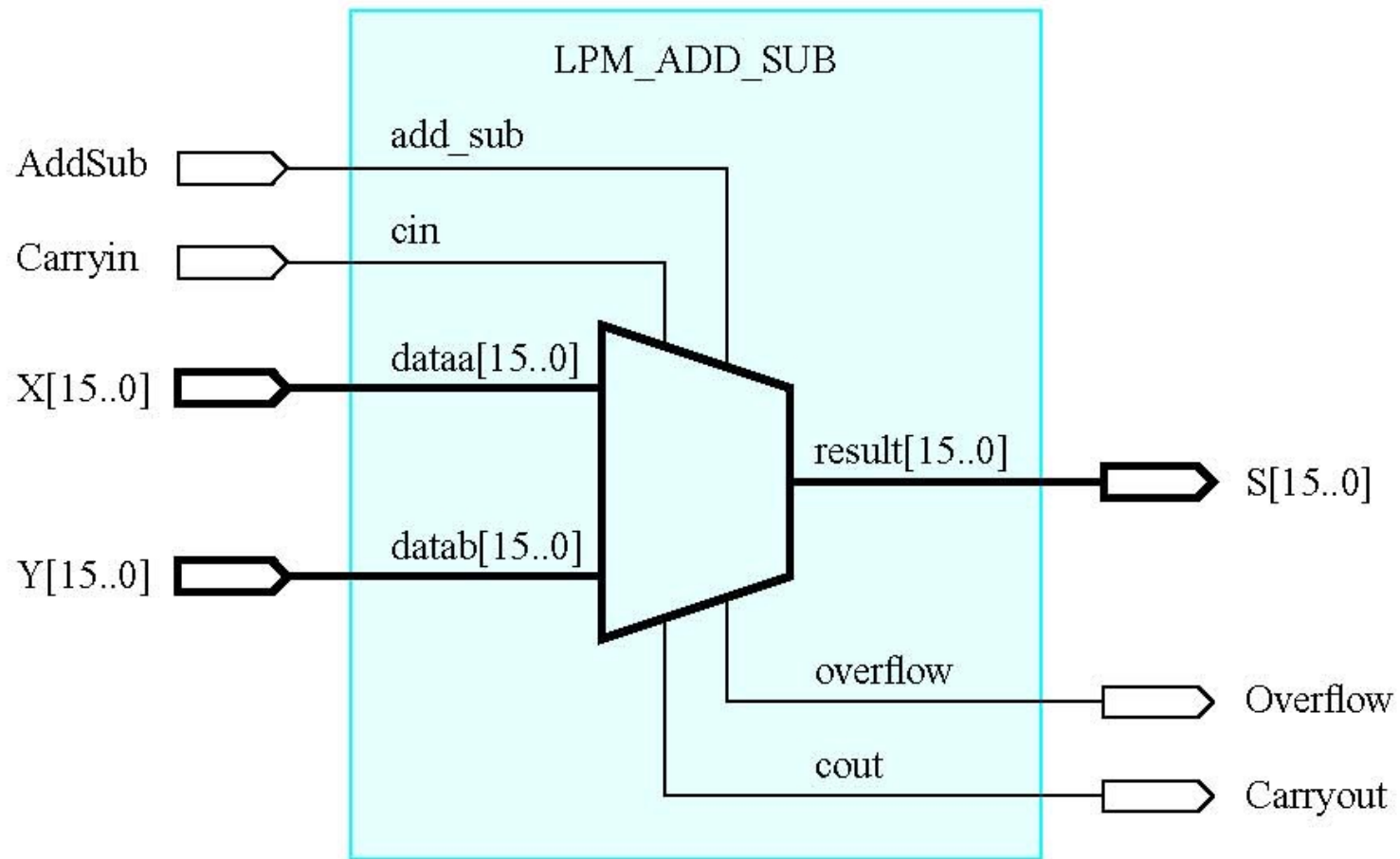
# Schematic using an LPM adder/subtractor



# Examples of Adder Implementation in VHDL

# VHDL code for the 1-Bit full-adder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( Cin, x, y : IN STD_LOGIC ;
          s, Cout : OUT STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;
```

# VHDL code for a four-bit adder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY adder4 IS
    PORT ( Cin : IN STD_LOGIC ;
          x3, x2, x1, x0 : IN STD_LOGIC ;
          y3, y2, y1, y0 : IN STD_LOGIC ;
          s3, s2, s1, s0 : OUT STD_LOGIC ;
          Cout          : OUT STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
    COMPONENT fulladd
        PORT ( Cin, x, y : IN STD_LOGIC ;
              s, Cout   : OUT STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        Cin => c3, Cout => Cout, x => x3, y => y3, s =>
s3 ) ;
END Structure ;
```

# Declaration of a package.

*(alternative style of code)*

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
PACKAGE fulladd_package IS
```

```
    COMPONENT fulladd
```

```
        PORT ( Cin, x, y      : IN STD_LOGIC ;
```

```
              s, Cout : OUT STD_LOGIC ) ;
```

```
    END COMPONENT ;
```

```
END fulladd_package ;
```

- A different way of specifying a four-bit adder.

Your Last Name has to be part of package name!

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (      Cin      : IN   STD_LOGIC ;
           x3, x2, x1, x0 : IN   STD_LOGIC ;
           y3, y2, y1, y0 : IN   STD_LOGIC ;
           s3, s2, s1, s0 : OUT  STD_LOGIC ;
           Cout  : OUT  STD_LOGIC ) ;
END adder4 ;
```

```
ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        Cin => c3, Cout => Cout, x => x3, y => y3, s => s3 ) ;
END Structure ;
```


# A four-bit adder defined using multibit signals

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (      Cin      : IN   STD_LOGIC ;
           X, Y : IN   STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           S      : OUT  STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           Cout   : OUT  STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

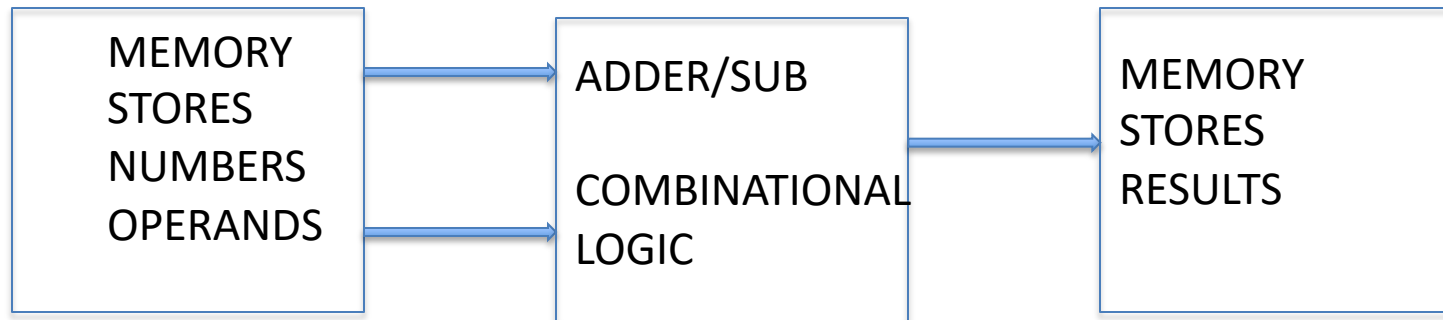ADDER/ SUB USAGE  
In the future lab  
**NOT IN THIS ONE**



READ FROM MEMORY

WRITE TO MEMORY