

Christopher Lall
CSc 342/343 Comp Org – Professor Gertner
ALU Lab Experiment
Due 4/10/22

Table of Contents

Objective: 3

Code: 3

Simulation/ModelSim: 13

Conclusion:..... 19

Objective:

The goal of this lab is to use an Instruction Register (IR), a 3-Port RAM (which accesses registers Rs, Rt, and Rd as needed), an Immediate Register for I-Format Instructions, a Data Memory (1-Port RAM), an ADD/SUB unit with flags overflow, negative, and zero, and finally a Bitwise Operation Unit integrated within the former unit to implement 16 MIPS Instructions in VHDL. Students must evaluate the validity of their design using ModelSim waveform simulation and compare the VHDL executed version of the MIPS instruction to its MARS equivalent after creating these instructions.

Code:

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Lall_RD is
5      generic (Lall_datawidth: integer := 32);
6      port (
7          Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
8          Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
9          Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
10 end Lall_RD;
11
12 architecture arch of Lall_RD is
13
14     signal Lall_memory: std_logic_vector(Lall_datawidth-1 downto 0);
15
16     begin
17         P1: process(Lall_clock, Lall_write)
18         begin
19             if(rising_edge(Lall_clock) and Lall_write = '1')
20             then Lall_memory <= Lall_content;
21             end if;
22         end process P1;
23
24         P2: process(Lall_read, Lall_enable, Lall_memory)
25         begin
26             if(Lall_read = '1' and Lall_enable = '1')
27             then Lall_result <= Lall_memory;
28             elsif(Lall_enable = '0')
29             then Lall_result <= (others => '0');
30             end if;
31         end process P2;
32     end arch;

```

Figure 1. RD register VHDL code

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Lall_RS is
5      generic (Lall_datawidth: integer := 32);
6      port (
7          Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
8          Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
9          Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
10 end Lall_RS;
11
12 architecture arch of Lall_RS is
13
14     signal Lall_memory: std_logic_vector(Lall_datawidth-1 downto 0);
15
16     begin
17         P1: process(Lall_clock, Lall_write)
18         begin
19             if(rising_edge(Lall_clock) and Lall_write = '1')
20             then Lall_memory <= Lall_content;
21             end if;
22         end process P1;
23
24         P2: process(Lall_read, Lall_enable, Lall_memory)
25         begin
26             if(Lall_read = '1' and Lall_enable = '1')
27             then Lall_result <= Lall_memory;
28             elsif(Lall_enable = '0')
29             then Lall_result <= (others => '0');
30             end if;
31         end process P2;
32     end arch;

```

Figure 2. RS register VHDL code

```

1  |library IEEE;
2  |use IEEE.std_logic_1164.all;
3
4  |entity Lall_RT is
5  |    generic (Lall_datawidth: integer := 32);
6  |    port (
7  |        Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
8  |        Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
9  |        Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
10 |    end Lall_RT;
11
12 |architecture arch of Lall_RT is
13 |
14 |    signal Lall_memory: std_logic_vector(Lall_datawidth-1 downto 0);
15 |
16 |    begin
17 |        P1: process(Lall_clock, Lall_write)
18 |        begin
19 |            if(rising_edge(Lall_clock) and Lall_write = '1')
20 |            then Lall_memory <= Lall_content;
21 |            end if;
22 |        end process P1;
23 |
24 |        P2: process(Lall_read, Lall_enable, Lall_memory)
25 |        begin
26 |            if(Lall_read = '1' and Lall_enable = '1')
27 |            then Lall_result <= Lall_memory;
28 |            elsif(Lall_enable = '0')
29 |            then Lall_result <= (others => '0');
30 |            end if;
31 |        end process P2;
32 |    end arch;

```

Figure 3. RT register VHDL code

Those are the three register files we had to create that IR register accesses based on the instructions. They are all 32-bit registers where RS and RT are used to store the two data values and RD writes the output signal once the arithmetic logic is complete.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_SIGNED.ALL;
4  use IEEE.numeric_std.ALL;
5
6  entity Lall_NBit_Addsub is
7      generic(n: integer := 32);
8      port( Lall_a, Lall_b: in std_logic_vector(n-1 downto 0);
9            Lall_sum: out std_logic_vector(n-1 downto 0);
10           Lall_cin: in std_logic;
11           Lall_op: in std_logic;
12           Lall_cout, Lall_o, Lall_N, Lall_Z: out std_logic);
13  end Lall_NBit_Addsub;
14
15  architecture nbitaddsub_behav of Lall_NBit_Addsub is
16      signal result: std_logic_vector(n-1 downto 0);
17      begin
18          result <= (Lall_a + Lall_b) WHEN (Lall_op = '0') ELSE (Lall_a - Lall_b);
19          Lall_cout <= '1' WHEN (Lall_op = '0' AND Lall_a(n-1) = Lall_b(n-1) AND result(n-1) /= Lall_a(n-1)) OR
20              (Lall_op = '1' AND Lall_a(n-1) /= Lall_b(n-1) AND result(n-1) /= Lall_a(n-1)) ELSE '0';
21          Lall_o <= '1' WHEN (Lall_op = '0' AND Lall_a(n-1) = Lall_b(n-1) AND result(n-1) /= Lall_a(n-1)) OR
22              (Lall_op = '1' AND Lall_a(n-1) /= Lall_b(n-1) AND result(n-1) /= Lall_a(n-1)) ELSE '0';
23          Lall_sum <= result;
24          Lall_N <= result(n-1);
25
26          process(result)
27          begin
28              if unsigned(result) = "0" then
29                  Lall_Z <= '1';
30              else
31                  Lall_Z <= '0';
32              end if;
33          end process;
34      end nbitaddsub_behav;
35

```

Figure 4. ADD/SUB VHDL code

When the opcode is 0 or 1 representing add and sub, we use the N-bit add/sub-component that we constructed in the previous experiments to perform adder/subtraction with overflow and negative flags.

```

1  |library IEEE;
2  |use IEEE.std_logic_1164.all;
3  |use IEEE.std_logic_signed.all;
4  |use IEEE.numeric_std.all;
5
6  |entity Lall_ALU is
7  |    generic(N: integer := 32);
8  |    port(
9  |        Lall_clk: in std_logic;
10 |        Lall_RS_i, Lall_RT_i, Lall_MDR_i: in std_logic_vector (N-1 downto 0); --32 bit register inputs
11 |        Lall_imm: in std_logic_vector (15 downto 0); --16 bit immediate
12 |        Lall_op: in std_logic_vector(3 downto 0); --Operation Code
13 |        Lall_RD_i: out std_logic_vector (N-1 downto 0); --32 bit register output
14 |        Lall_RD_out: out std_logic_vector (N-1 downto 0); --32 bit register output --TODO: HAVE RD OUTPUT
15 |        Lall_Z: out std_logic := '0'; --Zero flag
16 |        Lall_N: out std_logic := '0'; --Negative flag
17 |        Lall_O: out std_logic := '0'; --Overflow flag
18 |    end Lall_ALU;
19
20 |architecture arch of Lall_ALU is
21 |    signal cout, z_temp0, n_temp0, o_temp0, z_temp1, n_temp1, o_temp1, z_temp2, n_temp2, o_temp2, z_temp3, n_temp3, o_temp3,
22 |           z_temp4, n_temp4, o_temp4, z_temp5, n_temp5, o_temp5, z_temp6, n_temp6, o_temp6, mar_wren, mdr_wren : std_logic := '0';
23 |    signal temp0, temp1, temp2, temp3, temp4, temp5, temp6: std_logic_vector (N-1 downto 0);
24 |    signal RS_o, RT_o, RT_out, RD_i, ext_o, MAR_o, MDR_o: std_logic_vector (N-1 downto 0);
25 |    signal imm_o: std_logic_vector (15 downto 0);
26
27 |    component Lall_RD is
28 |        generic (Lall_datawidth: integer := 32);
29 |        port (
30 |            Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
31 |            Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
32 |            Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
33 |    end component;
34
35 |    component Lall_RT is
36 |        generic (Lall_datawidth: integer := 32);
37 |        port (
38 |            Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
39 |            Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
40 |            Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
41 |    end component;

```

Figure 5. ALU VHDL code part 1

```

42 |
43 |    component Lall_RS is
44 |        generic (Lall_datawidth: integer := 32);
45 |        port (
46 |            Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
47 |            Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
48 |            Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
49 |    end component;
50
51 |    component Lall_IMM16 is
52 |        generic (Lall_imm_size: integer := 16);
53 |        port (
54 |            Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
55 |            Lall_in: in std_logic_vector(Lall_imm_size-1 downto 0);
56 |            Lall_out: out std_logic_vector(Lall_imm_size-1 downto 0));
57 |    end component;
58
59 |    component Lall_Sign_Extend is
60 |        port( Lall_I: in std_logic_vector(15 downto 0);
61 |            Lall_Q: out std_logic_vector(31 downto 0));
62 |    end component;
63
64 |    component Lall_MAR is
65 |        generic (Lall_datawidth: integer := 32);
66 |        port (
67 |            Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
68 |            Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
69 |            Lall_ext: in std_logic_vector(Lall_datawidth-1 downto 0);
70 |            Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
71 |    end component;
72
73 |    component Lall_MDR is
74 |        generic (Lall_datawidth: integer := 32);
75 |        port (
76 |            Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
77 |            Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
78 |            Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
79 |    end component;

```

Figure 6. ALU VHDL code part 2

```

80
81 component Lall_NBit_AddSub is
82   generic(n: integer := 32);
83   port( Lall_a, Lall_b: in std_logic_vector(n-1 downto 0);
84         Lall_sum: out std_logic_vector(n-1 downto 0);
85         Lall_n: in std_logic;
86         Lall_op: in std_logic;
87         Lall_cout, Lall_o, Lall_N, Lall_Z: out std_logic);
88 end component;
89
90 component Lall_bitwise_op is
91   generic(N: integer := 32);
92   port(
93     Lall_IO, Lall_II, Lall_ext: in std_logic_vector (N-1 downto 0);
94     Lall_imm: in std_logic_vector (15 downto 0);
95     Lall_op: out std_logic_vector (3 downto 0);
96     Lall_Q: out std_logic_vector (N-1 downto 0);
97     Lall_Z: out std_logic := '0';
98     Lall_N: out std_logic := '0';
99     Lall_O: out std_logic := '0');
100 end component;
101
102 begin
103   -- Registers
104   RD: Lall_RD generic map (Lall_datawidth => 32) port map (Lall_clk, '1', '1', '1', RD_i, Lall_RD_o);
105   RS: Lall_RS generic map (Lall_datawidth => 32) port map (Lall_clk, '1', '1', '1', Lall_RS_i, RS_o);
106   RT: Lall_RT generic map (Lall_datawidth => 32) port map (Lall_clk, '1', '1', '1', Lall_RT_i, RT_o);
107   imm: Lall_IMM16 generic map (Lall_imm_size => 16) port map (Lall_clk, '1', '1', '1', Lall_imm, imm_o);
108   ext: Lall_Sign_Extend port map (Lall_imm, ext_o);
109   MAR: Lall_MAR generic map (Lall_datawidth => 32) port map (Lall_clk, '1', '1', '1', RS_o, ext_o, MAR_o);
110   MDR: Lall_MDR generic map (Lall_datawidth => 32) port map (Lall_clk, '1', '1', '1', Lall_MDR_i, MDR_o);
111
112   -- Operations
113   add: Lall_NBit_AddSub generic map (n => 32) port map (RS_o, RT_o, temp0, '0', '0', cout, o_temp0, n_temp0, z_temp0);
114   addi: Lall_NBit_AddSub generic map (n => 32) port map (RS_o, ext_o, temp1, '0', '0', cout, o_temp1, n_temp1, z_temp1);
115   addiu: Lall_NBit_AddSub generic map (n => 32) port map (RS_o, ext_o, temp2, '0', '0', cout, o_temp2, n_temp2, z_temp2);
116   addu: Lall_NBit_AddSub generic map (n => 32) port map (RS_o, RT_o, temp3, '0', '0', cout, o_temp3, n_temp3, z_temp3);
117   sub: Lall_NBit_AddSub generic map (n => 32) port map (RS_o, RT_o, temp4, '0', '1', cout, o_temp4, n_temp4, z_temp4);
118   subu: Lall_NBit_AddSub generic map (n => 32) port map (RS_o, RT_o, temp5, '0', '1', cout, o_temp5, n_temp5, z_temp5);
119   bit_op: Lall_bitwise_op generic map (N => 32) port map (RS_o, RT_o, ext_o, imm_o, Lall_op, temp6, z_temp6, n_temp6, o_temp6);
120
121
122

```

Figure 7. ALU VHDL code part 3

```

120
121
122   -- Assign results
123   P1: process(temp0, temp1, temp2, temp3, temp4, temp5, temp6)
124   begin
125     case Lall_op is
126       when "0000" => Lall_RD_out <= temp0; Lall_O <= o_temp0; Lall_N <= n_temp0; Lall_Z <= z_temp0;
127       when "0001" => RT_out <= temp1; Lall_O <= o_temp1; Lall_N <= n_temp1; Lall_Z <= z_temp1;
128       when "0010" => RT_out <= temp2; Lall_O <= '0'; Lall_N <= n_temp2; Lall_Z <= z_temp2;
129       when "0011" => Lall_RD_out <= temp3; Lall_O <= '0'; Lall_N <= n_temp3; Lall_Z <= z_temp3;
130       when "0100" => Lall_RD_out <= temp4; Lall_O <= o_temp4; Lall_N <= n_temp4; Lall_Z <= z_temp4;
131       when "0101" => Lall_RD_out <= temp5; Lall_O <= '0'; Lall_N <= n_temp5; Lall_Z <= z_temp5;
132       when "0110" | "1000" | "1001" | "1011" | "1100" | "1101" => Lall_RD_out <= temp6; Lall_O <= o_temp6; Lall_N <= n_temp6;
133       when "0111" | "1010" => RT_out <= temp6; Lall_O <= o_temp6; Lall_N <= n_temp6; Lall_Z <= z_temp6;
134       when "1110" => RT_out <= MAR_o;
135       when "1111" => RT_out <= MDR_o;
136       when others => Lall_RD_out <= x"00000000";
137     end case;
138   end process;
139 end arch;

```

Figure 8. ALU VHDL code part 4

The ALU file operates as a control unit, redirecting to other components based on the opcode to accomplish the logic operation. It redirects to the n-bit adder sub if the opcode is 0 or 1.


```

1  |library IEEE;
2  |use IEEE.std_logic_1164.all;
3  |use IEEE.std_logic_signed.all;
4  |use IEEE.numeric_std.all;
5
6  entity Lall_bitwise_op is
7      generic(N: integer := 32);
8      port(
9          Lall_I0, Lall_I1, Lall_ext: in std_logic_vector (N-1 downto 0); --32 bit register inputs
10         Lall_imm: in std_logic_vector (15 downto 0); --16 bit immediate
11         Lall_op: in std_logic_vector(3 downto 0); --Operation Code
12         Lall_Q: out std_logic_vector (N-1 downto 0); --32 bit register output
13         Lall_Z: out std_logic := '0'; --Zero flag (0 because bitwise op)
14         Lall_N: out std_logic := '0'; --Negative flag (0 because bitwise op)
15         Lall_O: out std_logic := '0'); --Overflow flag (0 because bitwise op)
16 end Lall_bitwise_op;
17
18 architecture arch of Lall_bitwise_op is
19     signal result: std_logic_vector (N-1 downto 0);
20
21 begin
22     p1: process(Lall_I0, Lall_I1, Lall_op, result)
23     begin
24         case Lall_op is
25             when "0110"=> result <= Lall_I0 AND Lall_I1; -- and
26             when "0111"=> result <= Lall_I0 AND Lall_ext; -- andi
27             when "1000"=> result <= Lall_I0 NOR Lall_I1; -- nor
28             when "1001"=> result <= Lall_I0 OR Lall_I1; -- or
29             when "1010"=> result <= Lall_I0 OR Lall_ext; --ori
30             when "1011"=> result <= std_logic_vector(shift_left(unsigned(Lall_I1), to_integer(unsigned(Lall_imm)))); -- sll
31             when "1100"=> result <= std_logic_vector(shift_right(unsigned(Lall_I1), to_integer(unsigned(Lall_imm)))); -- srl
32             when "1101"=> result <= std_logic_vector(shift_right(signed(Lall_I1), to_integer(unsigned(Lall_imm)))); -- sra
33             when others=> result <= x"00000000";
34         end case;
35
36         Lall_Q <= result;
37     end process;
38 end arch;

```

Figure 9. Bitwise op VHDL code

This component is called when OPCODE points to a bitwise operation, and it, along with the sign extender, conducts bitwise operations for two 32-bit values.

```

1  |library IEEE;
2  |use IEEE.std_logic_1164.all;
3  |use IEEE.numeric_std.all;
4
5  entity Lall_Sign_Extend is
6      port( Lall_I: in std_logic_vector(15 downto 0);
7            Lall_Q: out std_logic_vector(31 downto 0));
8  end Lall_Sign_Extend;
9
10 architecture arch of Lall_Sign_Extend is
11     signal extended: std_logic_vector(31 downto 0);
12
13 begin
14     Lall_Q <= std_logic_vector(resize(signed(Lall_I), extended'length));
15 end arch;

```

Figure 10. Sign Extender VHDL code

When we have a 32-bit value and a 16-bit IMM value, we use a sign extender to make the 16-bit value 32 bits by adding 0s to the tail of the 16-bit value. This allows us to complete the logic with two 32-bit values rather than one 32-bit and one 16-bit integer.

```

1  |library IEEE;
2  |use IEEE.std_logic_1164.all;
3
4  |entity Lall_IMM16 is
5  |    generic (Lall_imm_size: integer := 16);
6  |    port (
7  |        Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
8  |        Lall_in: in std_logic_vector(Lall_imm_size-1 downto 0);
9  |        Lall_out: out std_logic_vector(Lall_imm_size-1 downto 0));
10 |    end Lall_IMM16;
11
12 |architecture arch of Lall_IMM16 is
13 |
14 |    signal Lall_memory: std_logic_vector(Lall_imm_size-1 downto 0);
15 |
16 |    begin
17 |        P1: process(Lall_clock, Lall_write)
18 |        begin
19 |            if(rising_edge(Lall_clock) and Lall_write = '1')
20 |            then Lall_memory <= Lall_in;
21 |            end if;
22 |        end process P1;
23
24 |        P2: process(Lall_read, Lall_enable, Lall_memory)
25 |        begin
26 |            if(Lall_read = '1' and Lall_enable = '1')
27 |            then Lall_out <= Lall_memory;
28 |            elsif(Lall_enable = '0')
29 |            then Lall_out <= (others => '0');
30 |            end if;
31 |        end process P2;
32 |    end arch;

```

Figure 11. IMM16 VHDL code

This 16-bit immediate register that helps us perform the immediate operations with the help of sign extenders which turns the 16-bit to 32- bits.

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  use IEEE.STD_LOGIC_SIGNED.ALL;
4  use IEEE.numeric_std.ALL;
5
6  entity Lall_MAR is
7  generic (Lall_datawidth: integer := 32);
8  port (
9      Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
10     Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
11     Lall_ext: in std_logic_vector(Lall_datawidth-1 downto 0);
12     Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
13 end Lall_MAR;
14
15 architecture arch of Lall_MAR is
16
17     signal Lall_memory: std_logic_vector(Lall_datawidth-1 downto 0);
18
19     begin
20         P1: process(Lall_clock, Lall_write)
21         begin
22             if(rising_edge(Lall_clock) and Lall_write = '1')
23             then Lall_memory <= Lall_content + Lall_ext;
24             end if;
25         end process P1;
26
27         P2: process(Lall_read, Lall_enable, Lall_memory)
28         begin
29             if(Lall_read = '1' and Lall_enable = '1')
30             then Lall_result <= Lall_memory;
31             elsif(Lall_enable = '0')
32             then Lall_result <= (others => '0');
33             end if;
34         end process P2;
35     end arch;

```

Figure 12. MAR VHDL code

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  use IEEE.STD_LOGIC_SIGNED.ALL;
4  use IEEE.numeric_std.ALL;
5
6  entity Lall_MDR is
7      generic (Lall_datawidth: integer := 32);
8      port (
9          Lall_clock, Lall_write, Lall_read, Lall_enable: in std_logic;
10         Lall_content: in std_logic_vector(Lall_datawidth-1 downto 0);
11         Lall_result: out std_logic_vector(Lall_datawidth-1 downto 0));
12  end Lall_MDR;
13
14  architecture arch of Lall_MDR is
15
16      signal Lall_memory: std_logic_vector(Lall_datawidth-1 downto 0);
17
18  begin
19      P1: process(Lall_clock, Lall_write)
20      begin
21          if(rising_edge(Lall_clock) and Lall_write = '1')
22          then Lall_memory <= Lall_content;
23          end if;
24      end process P1;
25
26      P2: process(Lall_read, Lall_enable, Lall_memory)
27      begin
28          if(Lall_read = '1' and Lall_enable = '1')
29          then Lall_result <= Lall_memory;
30          elsif(Lall_enable = '0')
31          then Lall_result <= (others => '0');
32          end if;
33      end process P2;
34  end arch;

```

Figure 13. MDR VHDL code

Simulation/ModelSim:

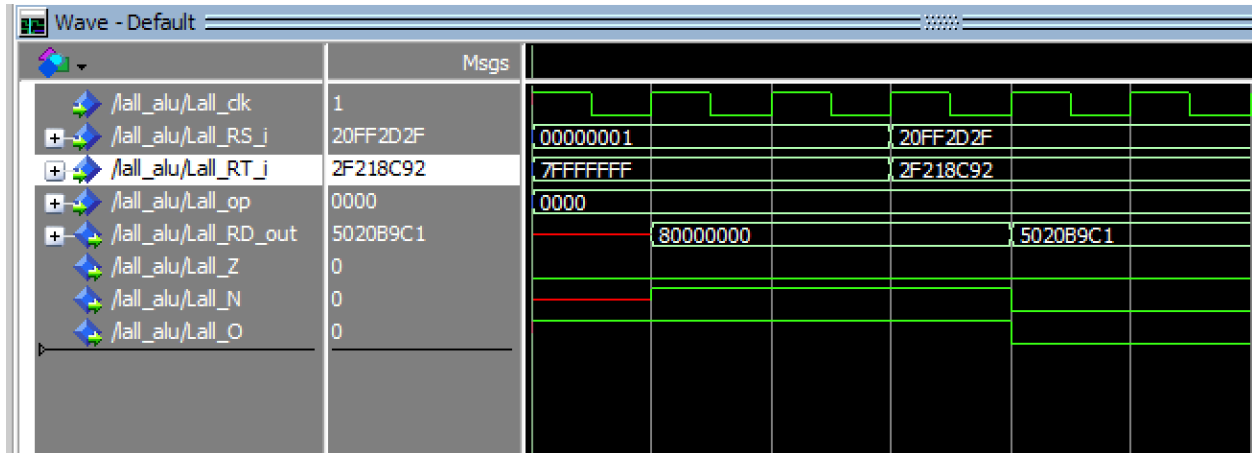


Figure 14. ADD waveform neg and overflow modelsim.

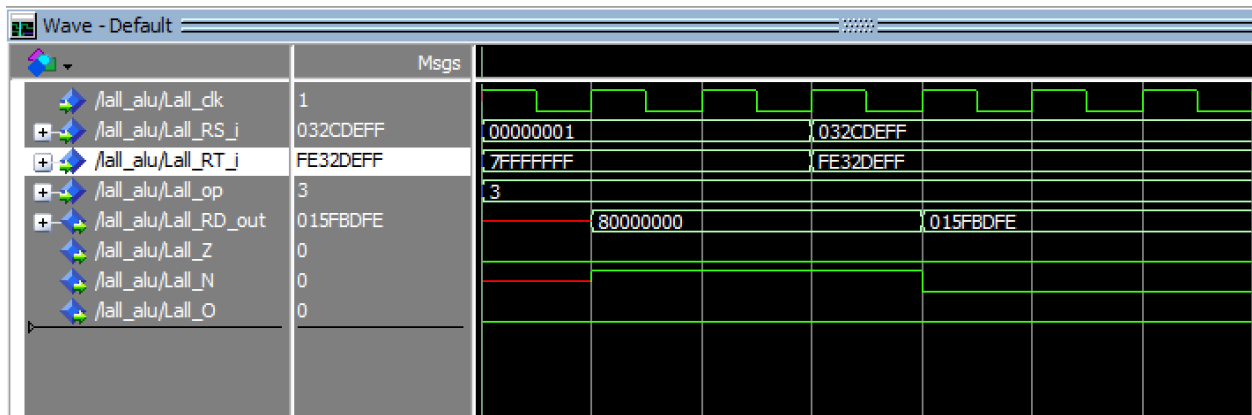


Figure 15. Add underflow waveform modelsim

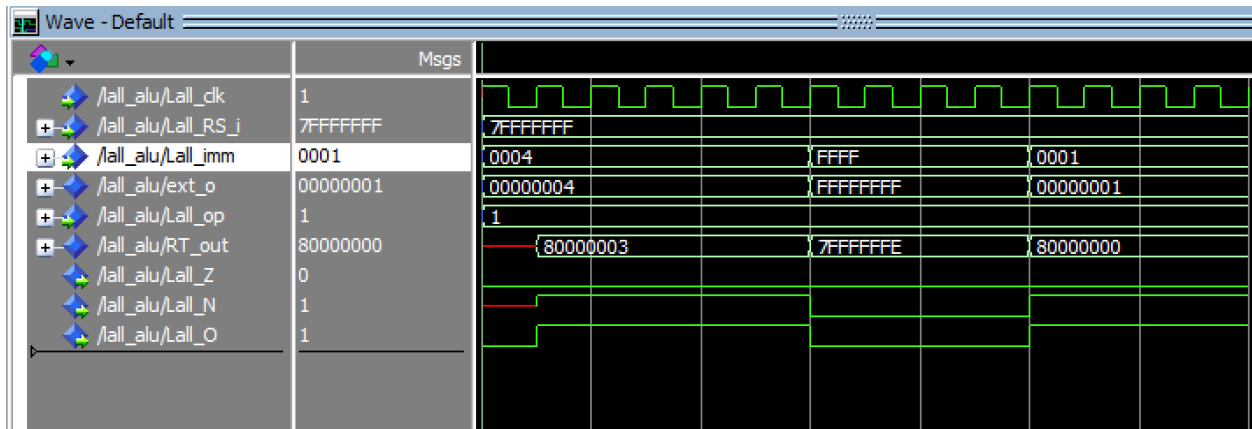


Figure 16. ADD with IMM ModelSim waveform

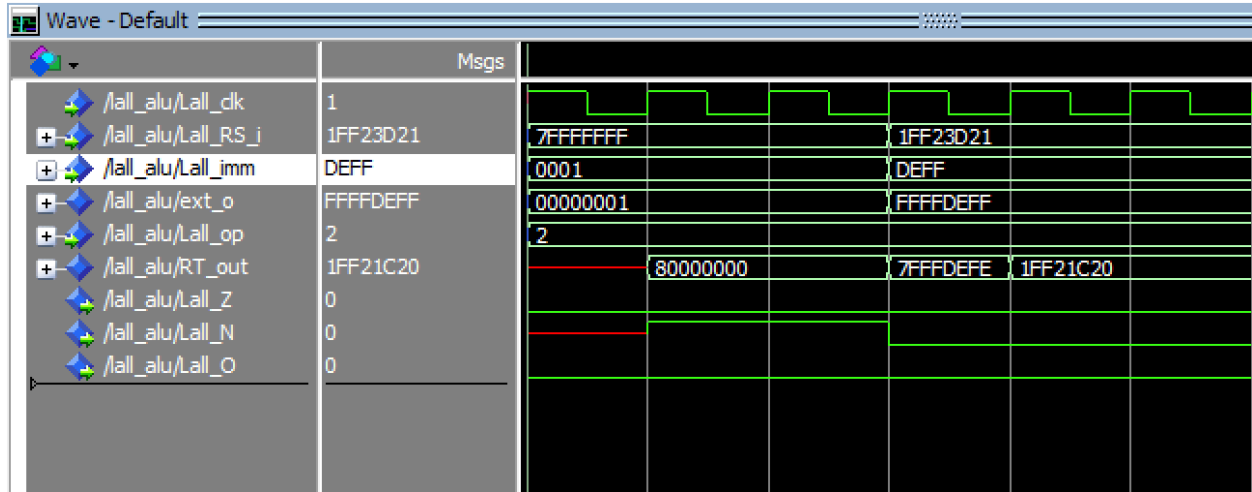


Figure 17. ADDIU IMM modelsim waveform

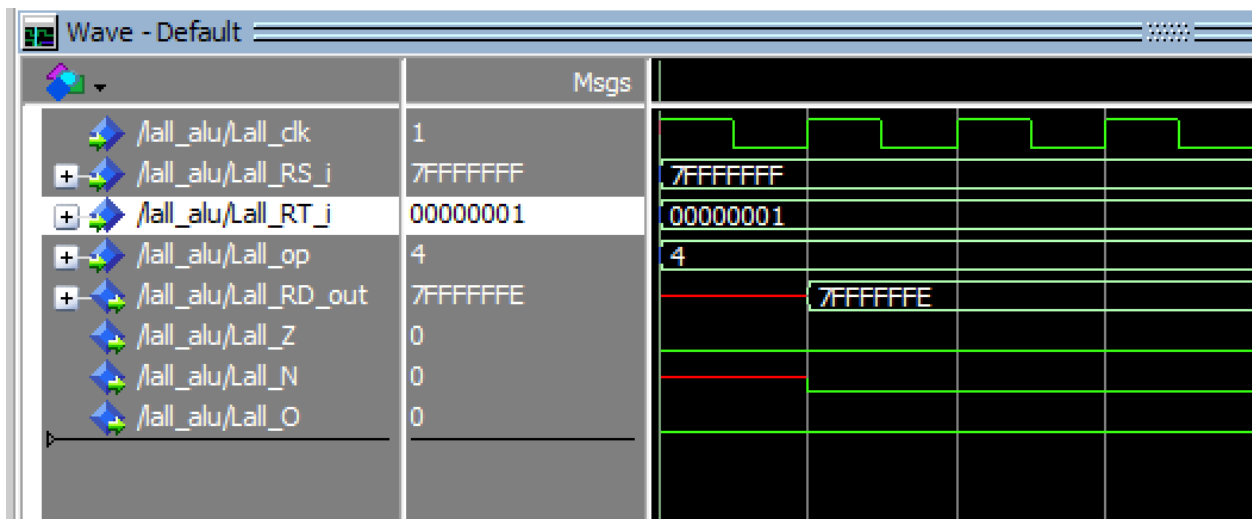


Figure 18. Subtraction of ALU modelsim waveform

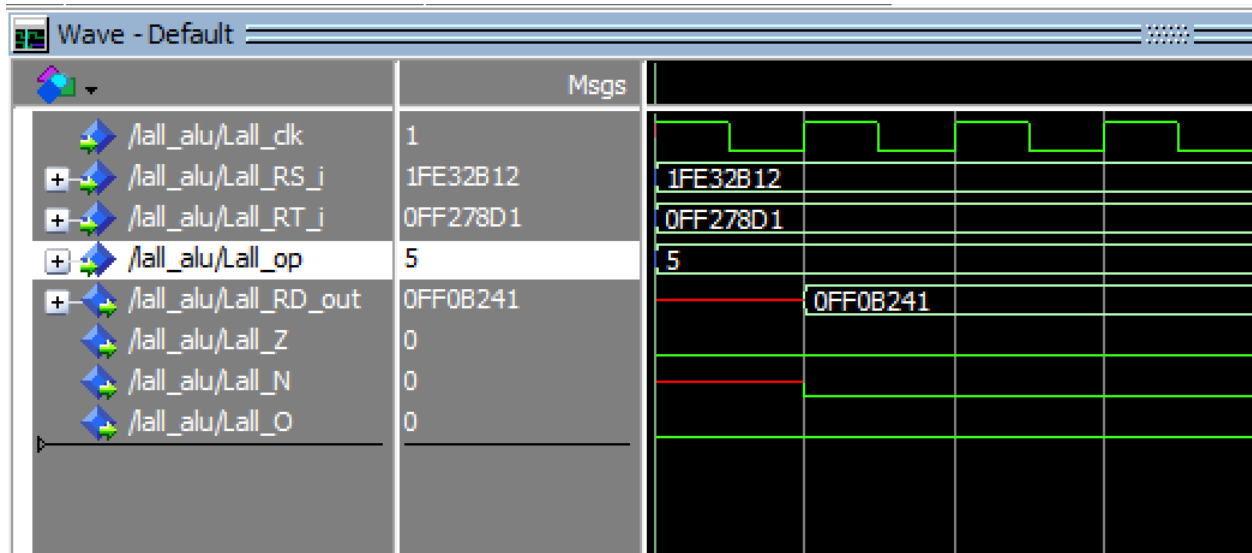


Figure 19. SUBU modelsim waveform

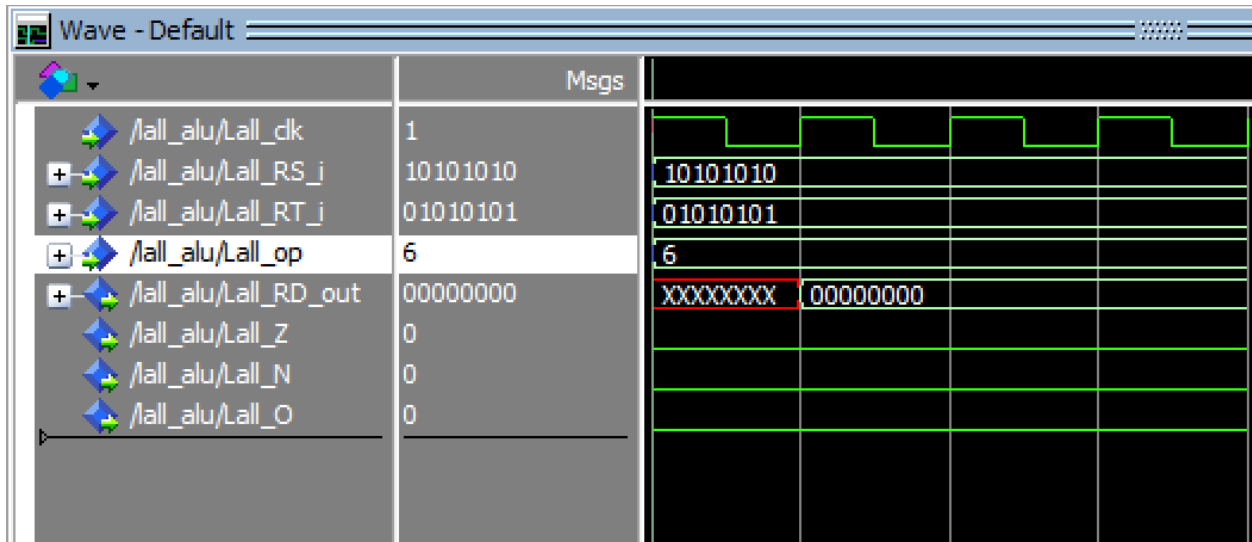


Figure 20. AND modelsim waveform

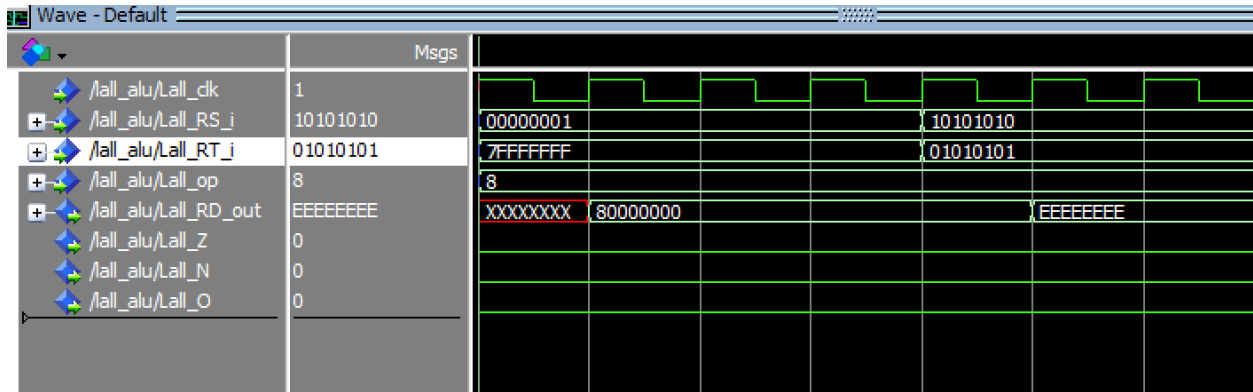


Figure 21. NOR modelsim waveform

 


Figure 22. OR modelsim waveform

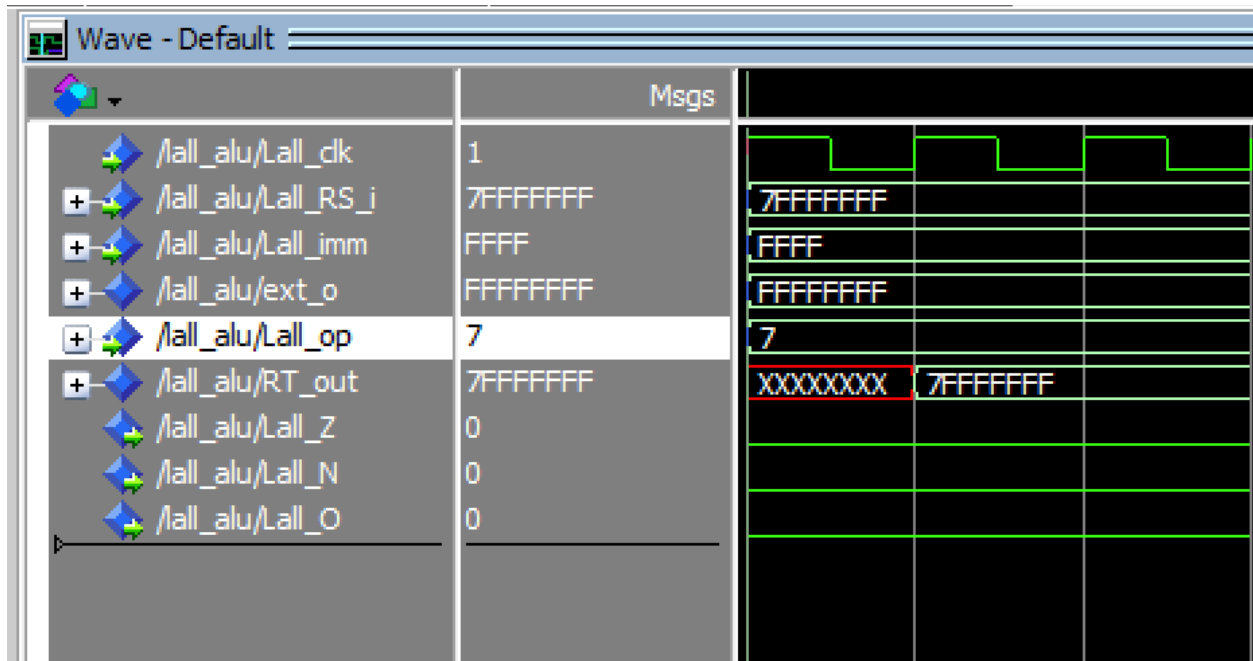


Figure 23. ADDI modelsim waveform

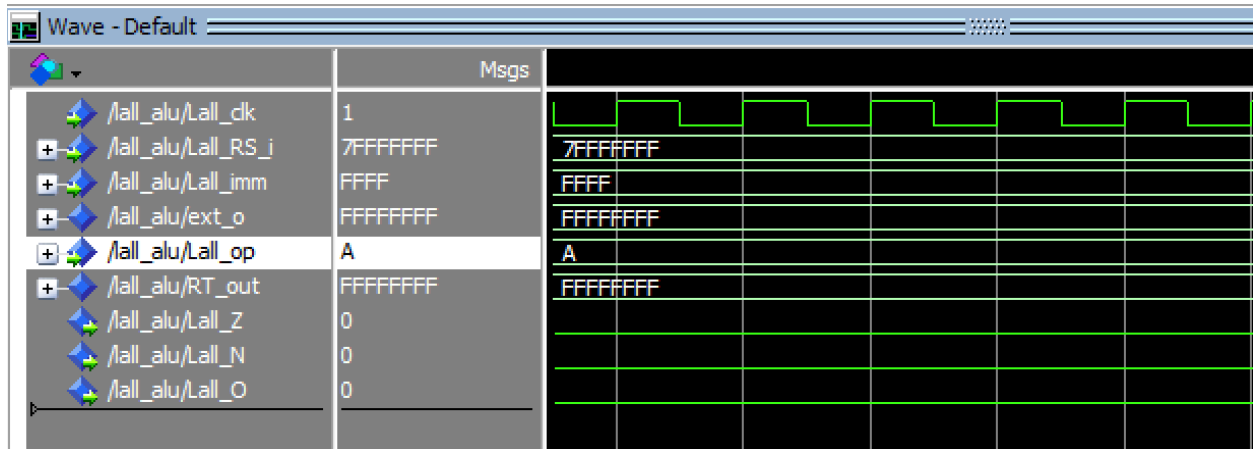


Figure 24. ORI modelsim waveform

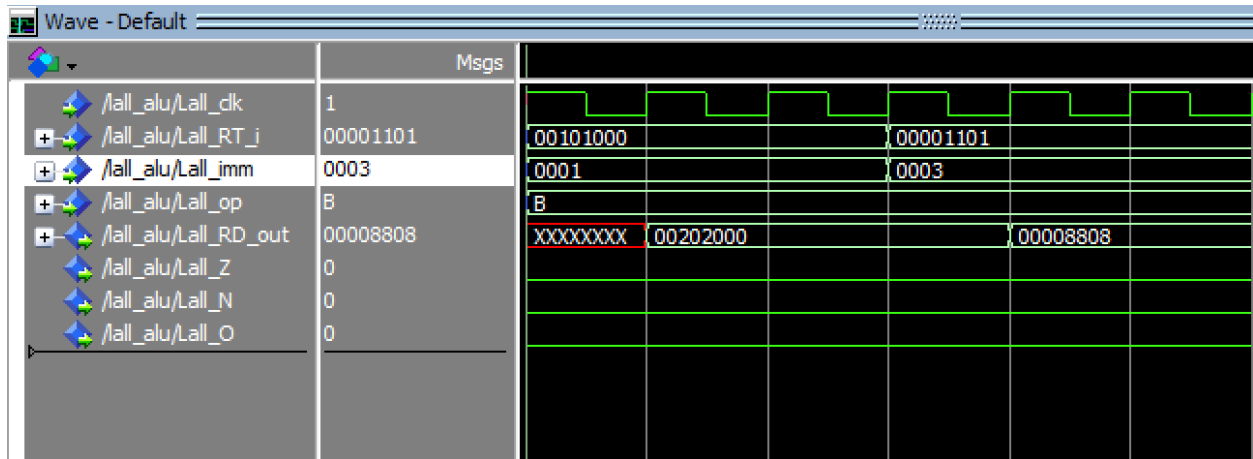


Figure 25. SLL modelsim waveform

 


Figure 26. SRL modelsim waveform

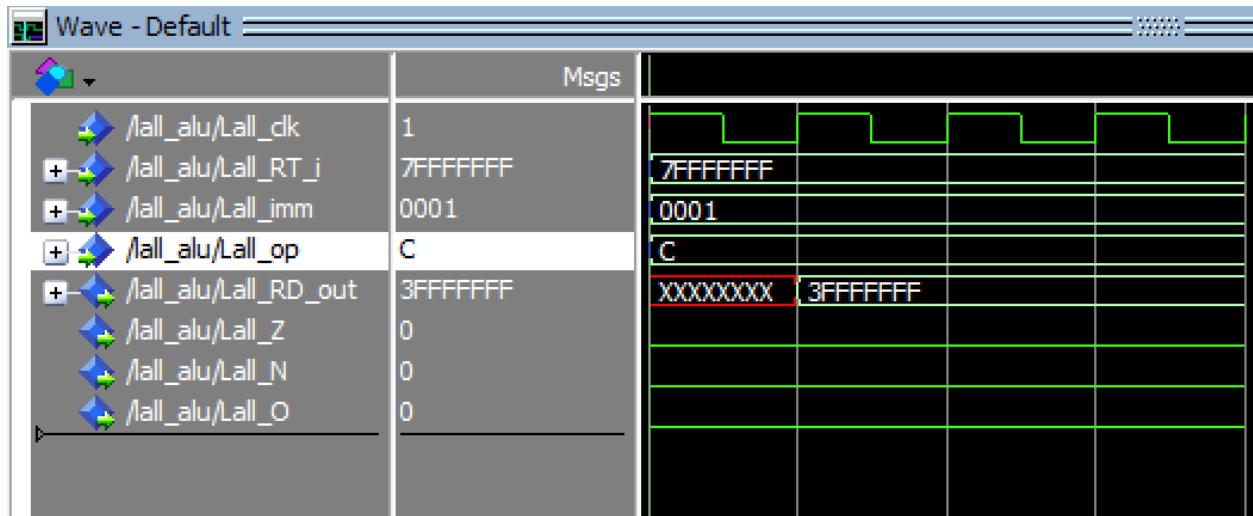


Figure 27. SRA modelsim waveform

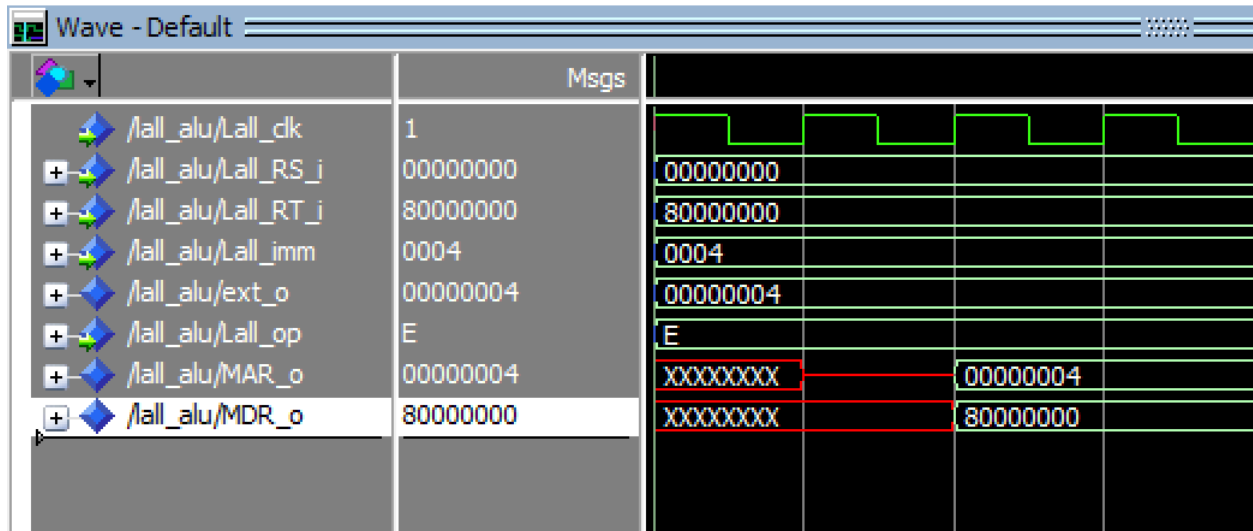


Figure 28. SW modelsim waveform

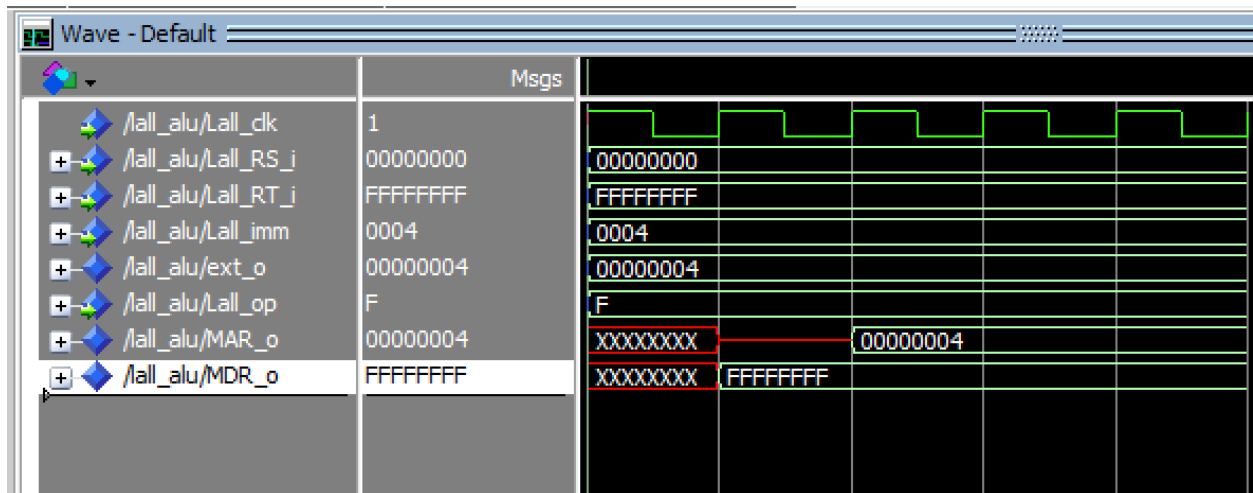


Figure 29. LW modelsim waveform

Conclusion:

We learned how to design an ALU unit capable of simulating the behavior of 16 MIPS instructions in both R-Format and I-Format formats. We learned how to create a data memory unit and how to utilize it to do operations like store and load words. We learnt how to configure and use access registers RS, RT, and RD for these instructions. Finally, we learned how arithmetic/logic operations are conducted among register values and how these values compare to the MIPS operations when these components are combined.