

Christopher Lall

Lab Experiment 4a, 4b, SRAM

CSc 342/343

Professor Gertner

Due 3/14/22

Table of Contents

4A Part 1.....	3
4A Part 2.....	5
4A Part 3.....	5
4B	5
SRAM.....	6

4A Part 1

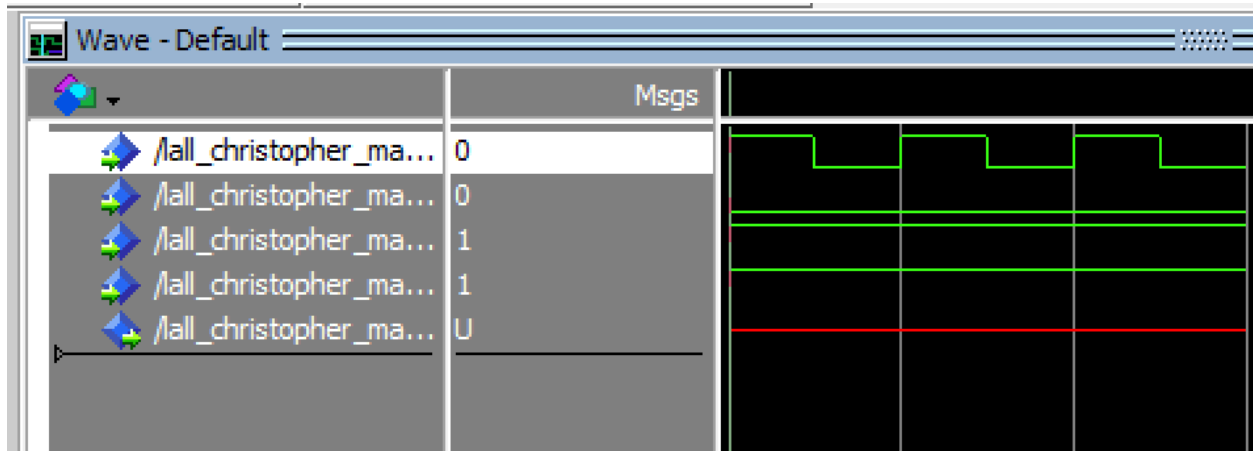


Figure 1. D on and off, Q redline.

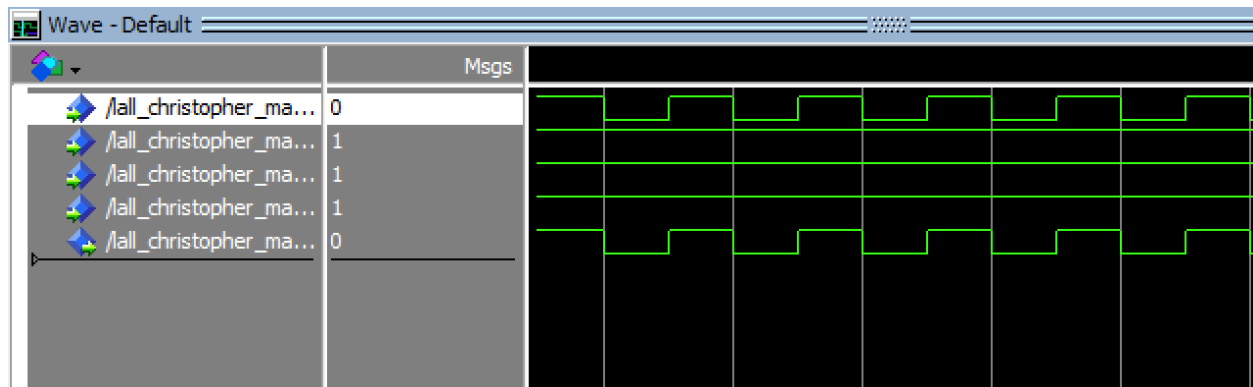


Figure 2. E forced to 1. Q follows D

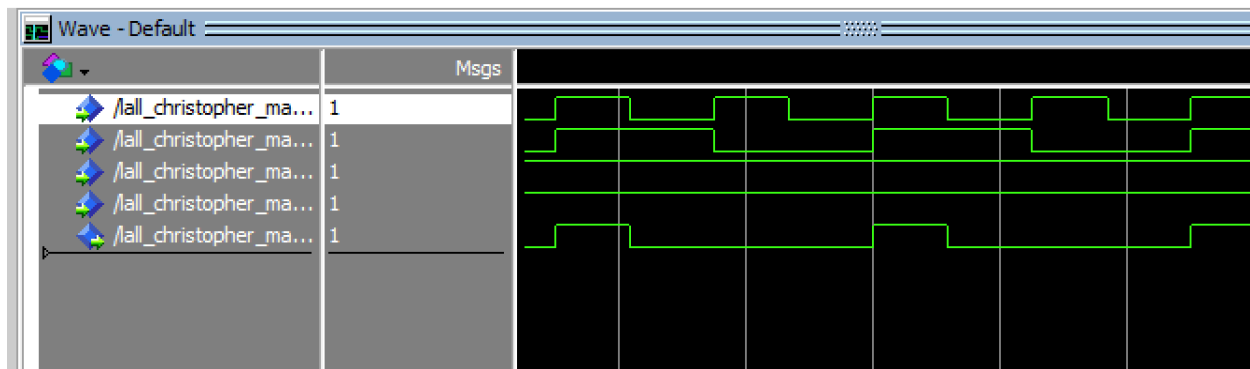


Figure 3. Q mirrors D

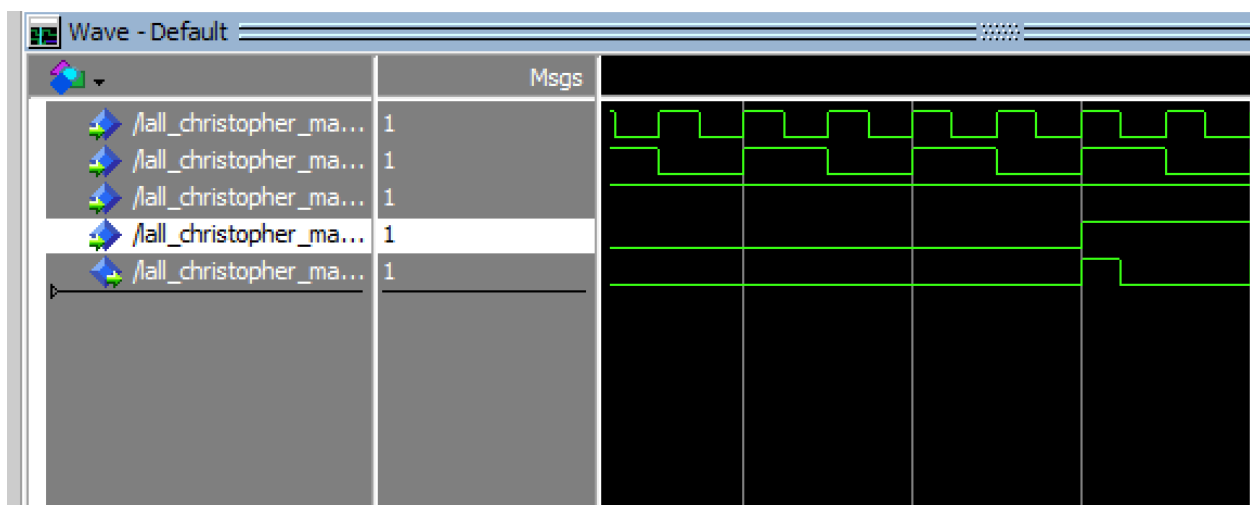


Figure 4. CLRN 0 to 1

4A Part 2

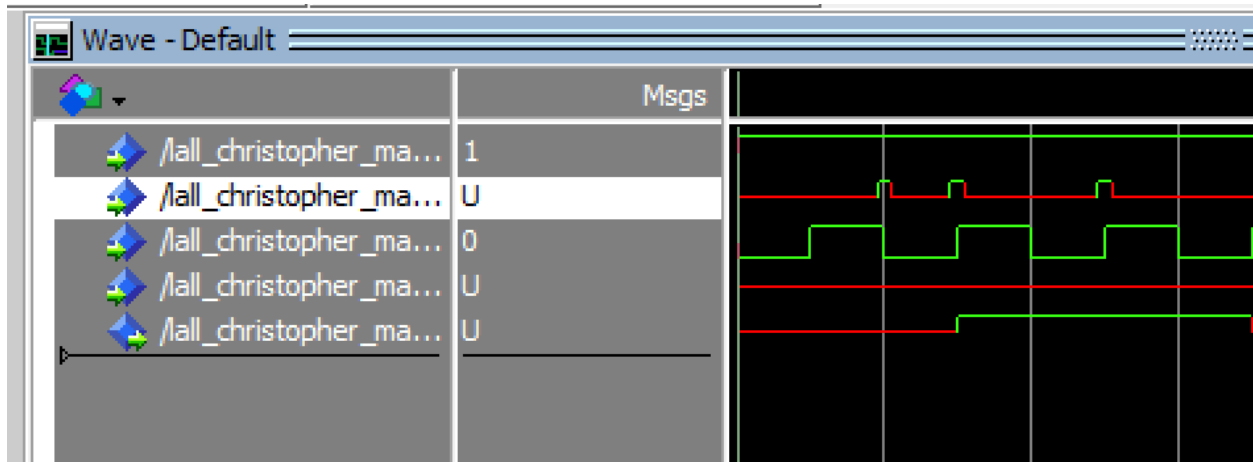


Figure 5. Master slave works exactly like d flip flop

4A Part 3

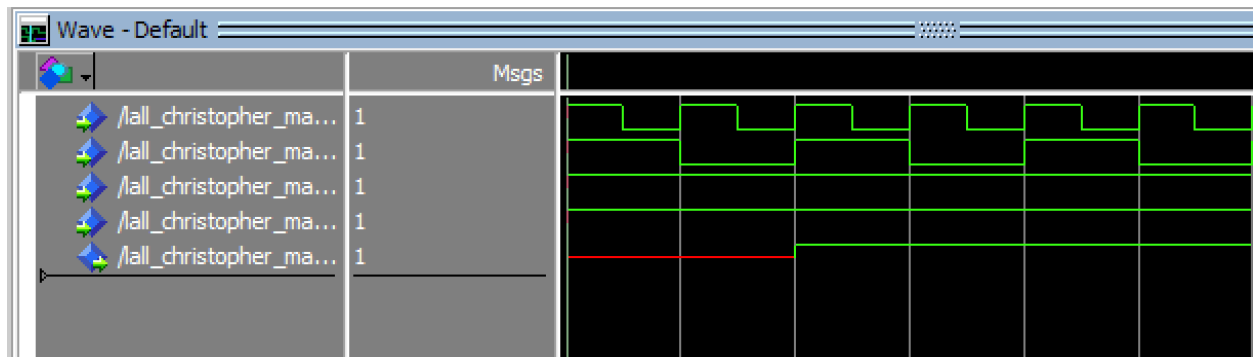


Figure 6. Edge twice the speed of D

4B

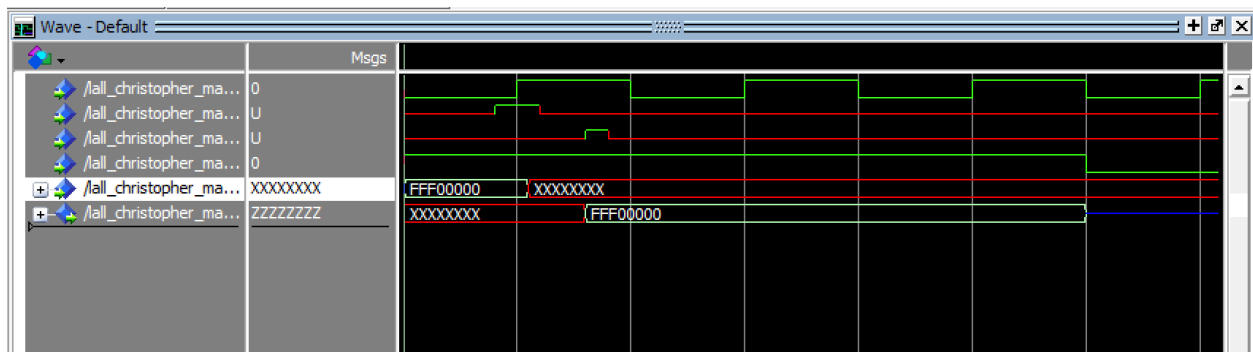


Figure 7. Storage and output display, chip enabling moves from 1 to 0 which changed output to undefined.

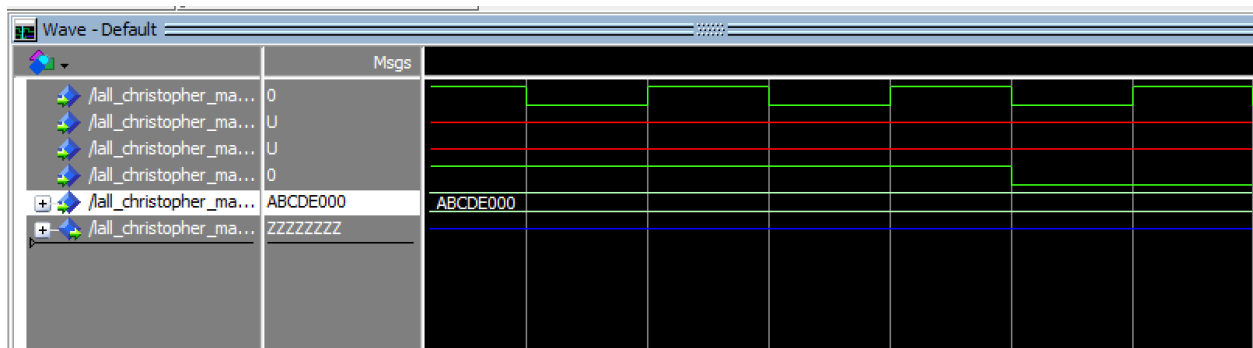


Figure 8. Same idea as example above, however, just my example of changing the hex value.

SRAM

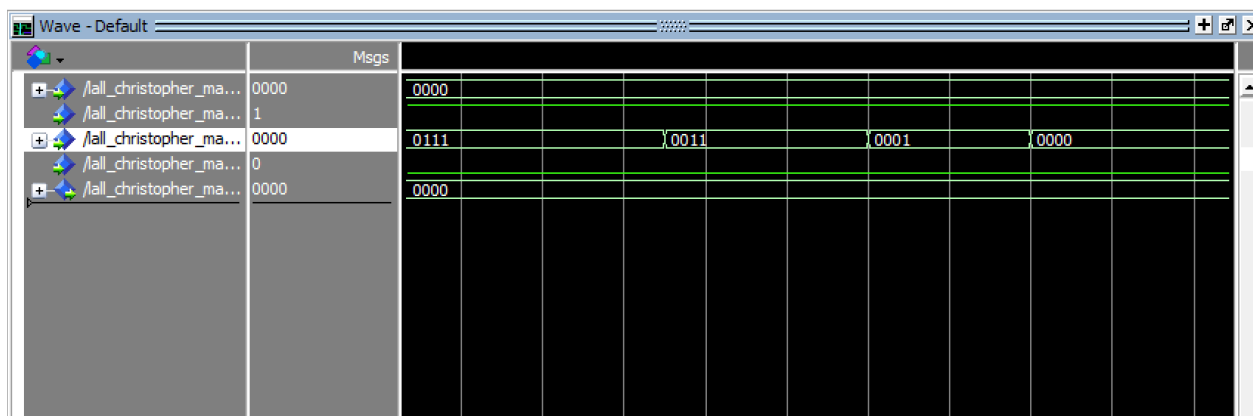


Figure 9. Sram waves